

TRANSISTOR TESTER

WITH a view to holding costs at a reasonable level and using ex-equipment devices where possible the circuit of Fig. 1 was developed to test transistors.

Used as a plug-in extension to an existing multimeter, the tester will measure I_{coe} from 0 to $30\mu A$ and 0 to $300\mu A$ and β from 0 to 120 and 0 to 300 at 5mA. The values of the components given are for a multimeter with a $30\mu A$, $1k\Omega$ movement, but calculations for other instruments are quite straightforward.

Heart of the unit is the constant current source, R3, R4, R5, D1, D2, which feeds a known I_b to the transistor under test. The choice of voltage for D1 and D2 is fairly restricted as it has to be high enough to overcome V_{be} variations but sufficiently low to allow a reasonable use of the battery supply. In the event, 6V seems a good compromise.

Neglecting a small I_{coe} , β is given by I_c/I_b , which gives

$$R_{base} = \frac{V_{effective}}{I_b} \text{ or } \frac{V_{eff} \times \beta}{I_c}$$

The voltage across the base resistance R_b is only the effective voltage V_{eff} of one diode as the forward voltage of the other is approximately equal to V_{be} . R3 is chosen such that it allows I_b to flow even at a low battery voltage but does not consume excessive power.

As constant alteration of meter setting is not attractive in such an application the flexibility is accommodated in the circuit of Fig. 1 and the meter is used on its most sensitive range. R9 protects overcurrent from flowing in the event of a shorted device. R10 shunts the still

protected meter up to $300\mu A$.

For leakage measurements S3 is open circuit and even though the base is connected to ground via D1 and D2 it is effectively open circuit.

R9 must be shorted for β measurements and R8 is used to shunt the meter to 5mA. In this position R6 gives some protection, limiting the current to about 15mA on short circuit. For a diode test R7 limits the current to 3mA.

For reliable operation the battery voltage should be greater than 7V and the battery should be capable of supplying 6mA.

For a transistor holder I used half an 8-pin d.i.l. socket soldered on a piece of Veroboard which in turn was Araldited to the top of a box containing the circuitry and switches.

S4 is connected so that with S4a open and S4b closed both h_{fe} and leakage measurements are at their least sensitive. The meter is less

likely to be overloaded if S4 is kept in this state and switched if needed.

S2 gives *npn* in position a, *pnp* in position b and battery test in position c. For diode testing the device to be tested is inserted in the anode and cathode sockets. If it conducts on *npn* then the anode and cathode terminals indicate actual terminations, if the reverse then the opposite connections apply.

The unit is not intended to be accurate beyond about 10 per cent but devices can be matched to about 2 per cent.

N. E. Thomas,
Oxford.

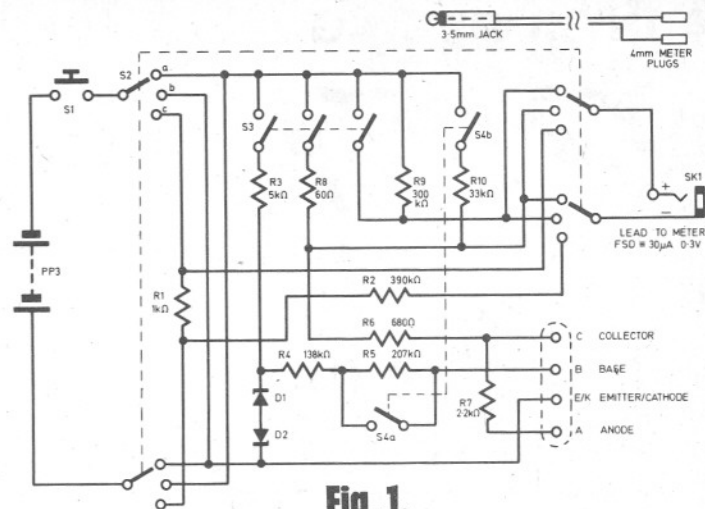


Fig. 1.

LIGHTING CONTROL MODIFICATIONS

SOME readers may find that the circuit used in the "Lighting Control Unit" (July 1973 issue) is not entirely suited to some salvaged components. In particular the transistor TR1.

If a silicon device is used in this position there is a danger of base-emitter breakdown due to reverse bias and this indeed occurred with two BC169C's used in the writer's circuit.

The insertion of protection diodes in the base leads has served to cure the problem quite easily and readily available OA81 devices were used. Equally, OA71 could be used.

A further modification to this useful circuit, shown in Fig. 1, is to include two controls for the original VR1 so as to obtain greater control over some of the effects.

J. Adams,
Oxford.

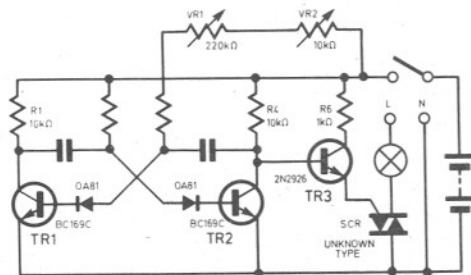


Fig. 1.

POINTS ARISING

P.E. ORION (January and February 1975)

In the components list the case was quoted as being GB3, this should be GB1.

The mains transformer SL8 can be obtained direct from Gardners Transformers Ltd. see Market Place page 234.

P.E. MINISONIC-3 (January 1975)

In the components list, for the H.F. Detector transistor, TR1 was not listed. This should be type BC184.

DIGITAL LEAF (January 1975)

See Market Place page 234.

MARINE SPEEDOMETER (February 1975)

Due to poor reproduction of Fig. 3 it is impossible to identify the breaks in the copperstrips of the Veroboard. Assuming the board is annotated from the top left corner, strips A to NN and holes 1 to 46, the breaks should be made at the following points: 26G, 9J, 12T, X38, CC10, DD10, EE10, FF10, HH19, II19, LL38.